

CS2052 Computer Architecture

Department of Computer Science and Engineering, University of Moratuwa

## **Lab 9-10 – Nanoprocessor Design Competition**

Group Name : Nanocache

<b>Group Members</b>	<b>Index Number</b>
R . A . N Sankalana	190564N
M . M Poorna S. Cooray	190110V
H .D .S Vidulanka	190646T

Prepared for : CS2052

Date of performance : 17 / 03 / 2021

Date of submission : 12 / 04 / 2021

## Contents

<b>Lab Tasks</b> .....	3
<b>Assembly Program</b> .....	3
<b>VHDL Codes for the NanoProcessor</b> .....	4
1. 4-bit Add/Subtract Unit.....	4
2. 3-bit Adder .....	6
3. 3-bit Program Counter .....	8
4. K-way b-bit Multiplexer .....	9
5. Register Bank.....	18
6. Program ROM.....	21
7. Instruction Decoder.....	22
8. NanoProcessor .....	24
<b>Timing Diagrams</b> .....	30
1. 4-bit Add/Subtract Unit.....	30
2. 3-bit Adder .....	32
3. 3-bit Program Counter .....	34
4. K-way b-bit Multiplexer .....	36
5. Register Bank.....	38
6. Program ROM.....	41
7. Instruction Decoder.....	42
8. NanoProcessor .....	44
<b>Conclusion</b> .....	46
<b>Contribution of Members</b> .....	46

## Lab Tasks

The main task of this lab is to design a 4-bit processor which is capable of executing a set of predefined instructions. The arithmetic unit of the processor only focuses on addition and subtraction. The processor comprises of the following key components.

- 4-bit Add/Subtract unit
- 3-bit adder
- 3-bit Program Counter (PC)
- k-way b-bit multiplexers
  - 2-way 3-bit multiplexer
  - 2-way 4-bit multiplexer
  - 8-way 4-bit multiplexer
- Register Bank
- Program ROM
- Instruction Decoder

The whole project was completed as a team where lab tasks were evenly divided among the team members.

## Assembly Program

This assembly program was written to calculate the sum of all integers between 1 and 3. According to the lab report output was mapped to the Register 7 in the register bank. And the final value of sum was saved in that register. In this code we create a loop from instruction 4 to 7, to decrement numbers from 3 to 1 and add to the R7 register. In instruction 7, always check if R0 for jump. But it is by default "0000" then always it comes to the instruction 7 it returns to the instruction 4. Then we create a terminating condition for that loop in instruction 6. It checks the value of R1 and if it is zero terminate the program.

### Assembly Code :

```
MOVI R7, 0      ; R7 ← 0
MOVI R1, 3      ; R1 ← 3
MOVI R2, 1      ; R2 ← 1
NEG  R2         ; R2 ← Neg R2
ADD  R7, R1     ; R7 ← R7 + R1
ADD  R1, R2     ; R1 ← R1 + R2
JZR  R1, 6      ; If R1 0 jump to 6
JZR  R0, 4      ; If R0 jump to 4
```

### Machine Code :

Instruction 0	"101110000000",
Instruction 1	"100010000011",
Instruction 2	"100100000001",
Instruction 3	"010100000000",
Instruction 4	"001110010000",
Instruction 5	"000010100000",
Instruction 6	"110010000110",
Instruction 7	"110000000100"

## VHDL Codes for the NanoProcessor

### 1. 4-bit Add/Subtract Unit

4-bit adder-subtractor can add and subtract 4-bit binary numbers. A: A0, A1, A2, A3 and B: B0, B1, B2, B3 and Calctrl are the inputs of the adder subtractor. The circuit consists of 4 full adders to perform operations of 4-bit numbers. Calctrl holds the binary value which determines the operation is addition or subtraction.

#### VHDL code for 4-bit add/sub unit.

```
entity Adder_Subtractor is
Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
      B : in STD_LOGIC_VECTOR (3 downto 0);
      CalCtrl : in STD_LOGIC;
      C_out : out STD_LOGIC;
      Overflow : out STD_LOGIC;
      Zero : out STD_LOGIC;
      S : out STD_LOGIC_VECTOR (3 downto 0));
end Adder_Subtractor;

architecture Behavioral of Adder_Subtractor is
component Full_Adder is
port ( A: in std_logic;
      B: in std_logic;
      C_in: in std_logic;
      Sum: out std_logic;
      C_out: out std_logic);
end component;
```

```

SIGNAL B_in, S_out : std_logic_vector(3 downto 0);
SIGNAL FA0_S, FA0_C, FA1_S, FA1_C, FA2_S, FA2_C, FA3_S, FA3_C : std_logic;

begin
    B_in(0) <= B(0) XOR CalCtrl;
    B_in(1) <= B(1) XOR CalCtrl;
    B_in(2) <= B(2) XOR CalCtrl;
    B_in(3) <= B(3) XOR CalCtrl;

    FA_0 : Full_Adder
        port map ( A => A(0),
                   B => B_in(0),
                   C_in => CalCtrl,
                   Sum => S_out(0),
                   C_Out => FA0_C);

    FA_1 : Full_Adder
        port map (A => A(1),
                   B => B_in(1),
                   C_in => FA0_C,
                   Sum => S_out(1),
                   C_Out => FA1_C);

    FA_2 : Full_Adder
        port map (A => A(2),
                   B => B_in(2),
                   C_in => FA1_C,
                   Sum => S_out(2),
                   C_Out => FA2_C);


    FA_3 : Full_Adder
        port map (A => A(3),
                   B => B_in(3),
                   C_in => FA2_C,
                   Sum => S_out(3),
                   C_Out => C_out);

    S(0) <= S_out(0);
    S(1) <= S_out(1);
    S(2) <= S_out(2);
    S(3) <= S_out(3);
    Overflow <= (A(3) XNOR (CalCtrl XOR B(3))) AND (A(3) XOR S_out(3));
    Zero <= not (S_out(0) or S_out(1) or S_out(2) or S_out(3));

end Behavioral;

```
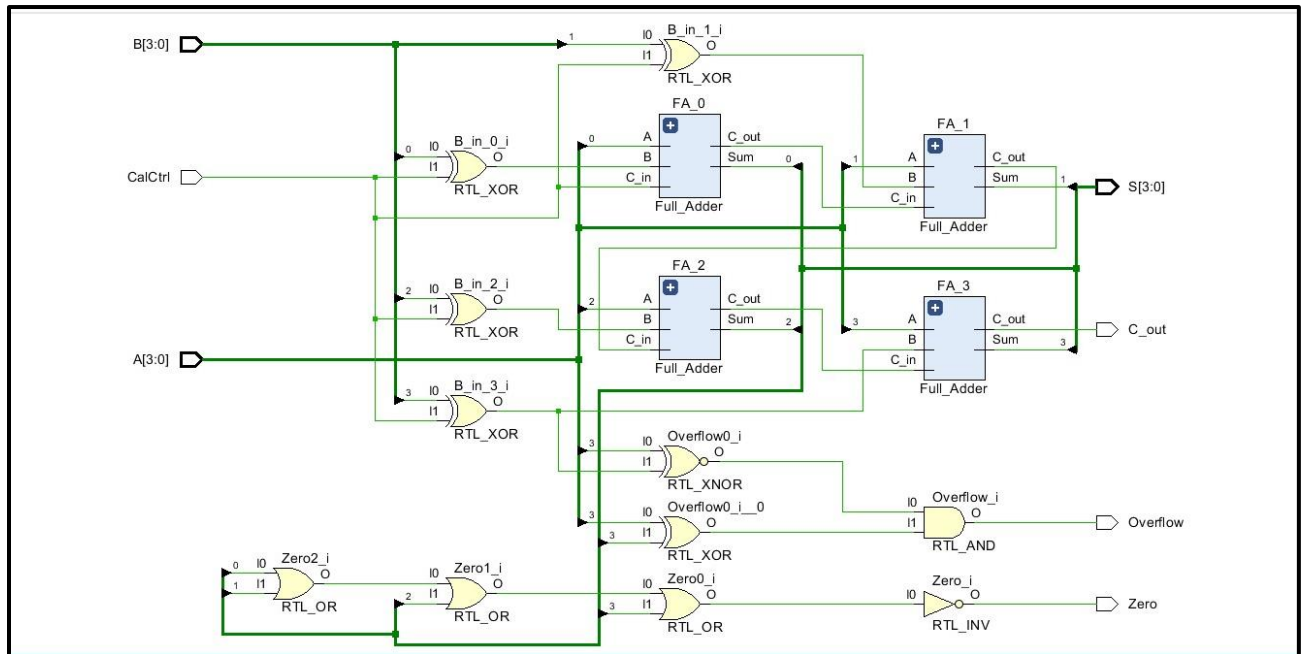
## RTL Schematic Diagram for add/sub unit



## 2. 3-bit Adder

3-bit adder, with an input and an output, is used to increment the program counter. The component is implemented using the half adder which was designed in Lab 3.

### Code for 3 – bit Adder

```
entity Adder_3_bit is
  Port ( TBA_in : in STD_LOGIC_VECTOR (2 downto 0);
        TBA_out : out STD_LOGIC_VECTOR (2 downto 0));
end Adder_3_bit;
```

architecture Behavioral of Adder\_3\_bit is

component HA

```
  Port ( A : in STD_LOGIC;
        B : in STD_LOGIC;
        S : out STD_LOGIC;
        C : out STD_LOGIC);
```

end component;


```
SIGNAL C_0 , C_1: std_logic;
```

```

begin
--adds one to the input
HA_0: HA
  Port map
    ( A => TBA_in(0),
      B => '1',
      S => TBA_out(0),
      C => C_0);
HA_1: HA
  Port map
    ( A => TBA_in(1),
      B => C_0,
      S => TBA_out(1),
      C => C_1);
HA_2: HA
  Port map
    ( A => TBA_in(2),
      B => C_1,
      S => TBA_out(2));
end Behavioral;

```
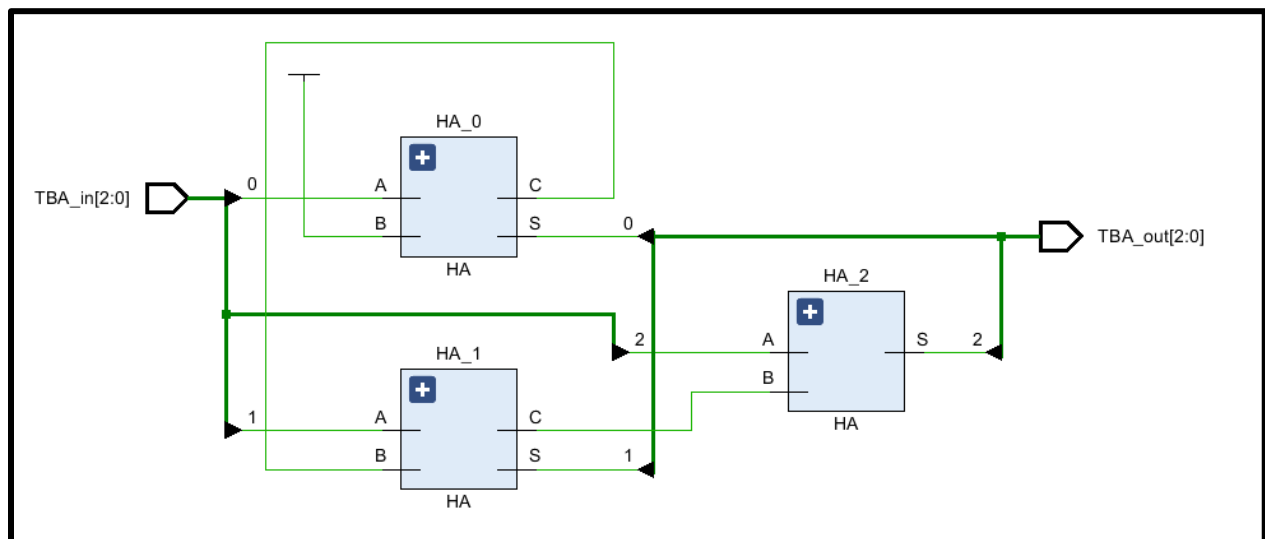
### RTL Schematic Diagram of 3 – bit Adder



### 3. 3-bit Program Counter

Program counter keeps track of the instruction address that is being executing at the current moment by the processor. The counter can be set to 0 by the reset button. Hence D flip flops from the Lab 5 are used here.

#### Code for Program Counter

```
entity ProgramCounter is
  Port ( I_in : in STD_LOGIC_VECTOR (2 downto 0);
        Clk : in STD_LOGIC;
        Res : in STD_LOGIC;
        I_out : out STD_LOGIC_VECTOR (2 downto 0));
end ProgramCounter;
architecture Behavioral of ProgramCounter is
  component D_FF
    Port ( D : in STD_LOGIC;
          Res : in STD_LOGIC;
          Clk : in STD_LOGIC;
          Q : out STD_LOGIC;
          Qbar : out STD_LOGIC);
  end component;

  begin
    D_FF_0: D_FF
      port map(
        D => I_in(0),
        Res=>Res,
        Clk=>Clk,
        Q=>I_out(0));


    D_FF_1: D_FF
      port map(
        D => I_in(1),
        Res=>Res,
        Clk=>Clk,
        Q=>I_out(1));

    D_FF_2: D_FF
      port map(
        D => I_in(2),
        Res=>Res,
        Clk=>Clk,
        Q=>I_out(2));

  end Behavioral;
```


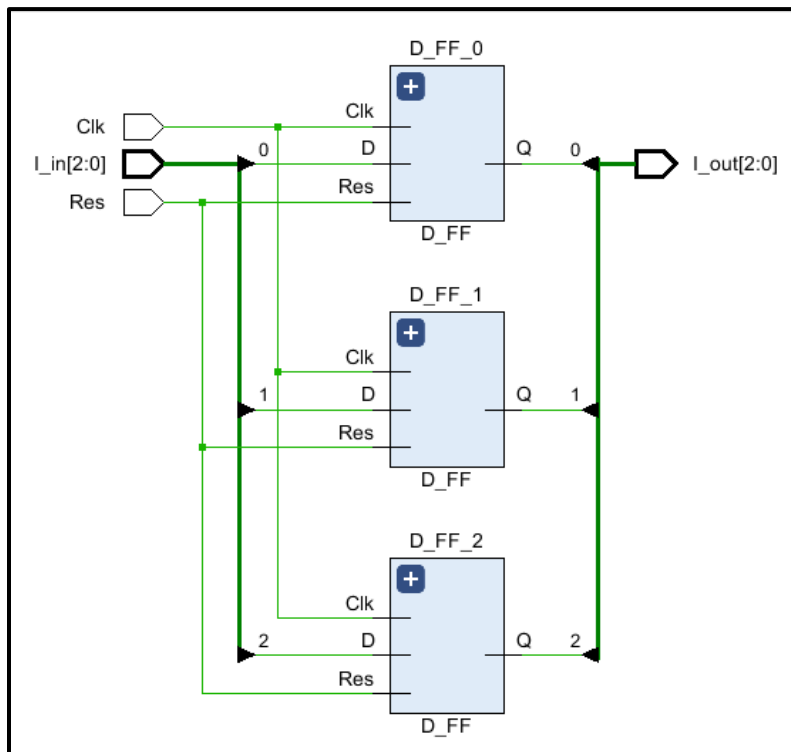
## RTL Schematic Diagram of 3-bit Program Counter



## 4. K-way b-bit Multiplexer

- There is main two ways to make a k-way b-bit multiplexers.
- In this lab we used Try state buffers to implement k-way b-bit multiplexers.
- To create that multiplexers only we need a decoder and “k” number of try state buffers.
- To make Nano processor we had to create 2-way 3-bit Multiplexer, 2-way 4-bit Multiplexer and 8-way 4-bit multiplexers.
- 2-way 3-bit mux used to select the jump address bus when jump flag raise otherwise it select the adder 3-bit output path.
- 2-way 3-bit mux used to select the Immediate Load when the Load select is high otherwise it selects the result bus of ALU.
- 8-way 4-bit mux is used to select the correct register when we input the address of it.

### Code for Try State Buffer


```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Try_State_Buffer_4_bit is
    Port ( Data_In : in STD_LOGIC_VECTOR (3 downto 0);
          EN : in STD_LOGIC;
          Data_Out : out STD_LOGIC_VECTOR (3 downto 0));
end Try_State_Buffer_4_bit;

architecture Behavioral of Try_State_Buffer_4_bit is

begin
    Data_Out <= Data_In when (EN = '1') else "ZZZZ";
end Behavioral;
```
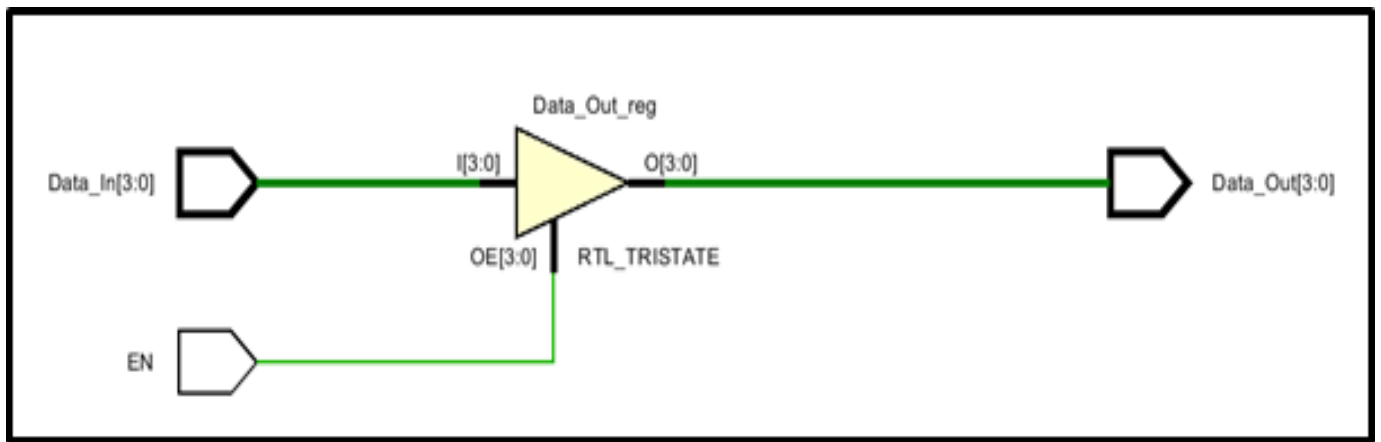
### RTL Schematic Diagram of Try State Buffer



- ❖ The implementation of all k-way b-bit multiplexers are same . the VHDL codes of all multiplexers are below.

### Code for 8-way 4-bit Multiplexer

```

entity Mux_8_way_4_bit is
  Port ( Reg0 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg1 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg2 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg3 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg4 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg5 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg6 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg7 : in STD_LOGIC_VECTOR (3 downto 0);
        EN : in STD_LOGIC;
        Reg_Sel : in STD_LOGIC_VECTOR (2 downto 0);
        Out_Val : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_8_way_4_bit;
architecture Behavioral of Mux_8_way_4_bit is
  --add a decoder to enable registers separately
  component Decoder_3_to_8
    Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR (7 downto 0));
  end component;
  --add a try state buffer to throw the correct input to common bus after enabling correct try state buffer
  component Try_State_Buffer_4_bit
    Port ( Data_In : in STD_LOGIC_VECTOR (3 downto 0);
          EN : in STD_LOGIC;
          Data_Out : out STD_LOGIC_VECTOR (3 downto 0));
  end component;
  Signal Common_Data_Bus : STD_LOGIC_VECTOR (3 downto 0);
  signal RegSel :STD_LOGIC_VECTOR (7 downto 0);

begin
  --decode the input register and select correct try state buffer
  Decoder: Decoder_3_to_8
    port map (
      I => Reg_Sel,
      EN => EN,
      Y => RegSel );

  Reg_0: Try_State_Buffer_4_bit
    port map(
      Data_In => Reg0,
      EN => RegSel(0),

```

```

        Data_Out => Common_Data_Bus );
Reg_1: Try_State_Buffer_4_bit
port map(
    Data_In => Reg1,
    EN => RegSel(1),
    Data_Out => Common_Data_Bus );

Reg_2: Try_State_Buffer_4_bit
port map(
    Data_In => Reg2,
    EN => RegSel(2),
    Data_Out => Common_Data_Bus );

Reg_3: Try_State_Buffer_4_bit
port map(
    Data_In => Reg3,
    EN => RegSel(3),
    Data_Out => Common_Data_Bus );

Reg_4: Try_State_Buffer_4_bit
port map(
    Data_In => Reg4,
    EN => RegSel(4),
    Data_Out => Common_Data_Bus );

Reg_5: Try_State_Buffer_4_bit
port map(
    Data_In => Reg5,
    EN => RegSel(5),
    Data_Out => Common_Data_Bus );


Reg_6: Try_State_Buffer_4_bit
port map(
    Data_In => Reg6,
    EN => RegSel(6),
    Data_Out => Common_Data_Bus );

Reg_7: Try_State_Buffer_4_bit
port map(
    Data_In => Reg7,
    EN => RegSel(7),
    Data_Out => Common_Data_Bus );
--output common bus
Out_Val <= Common_Data_Bus;

end Behavioral;

```
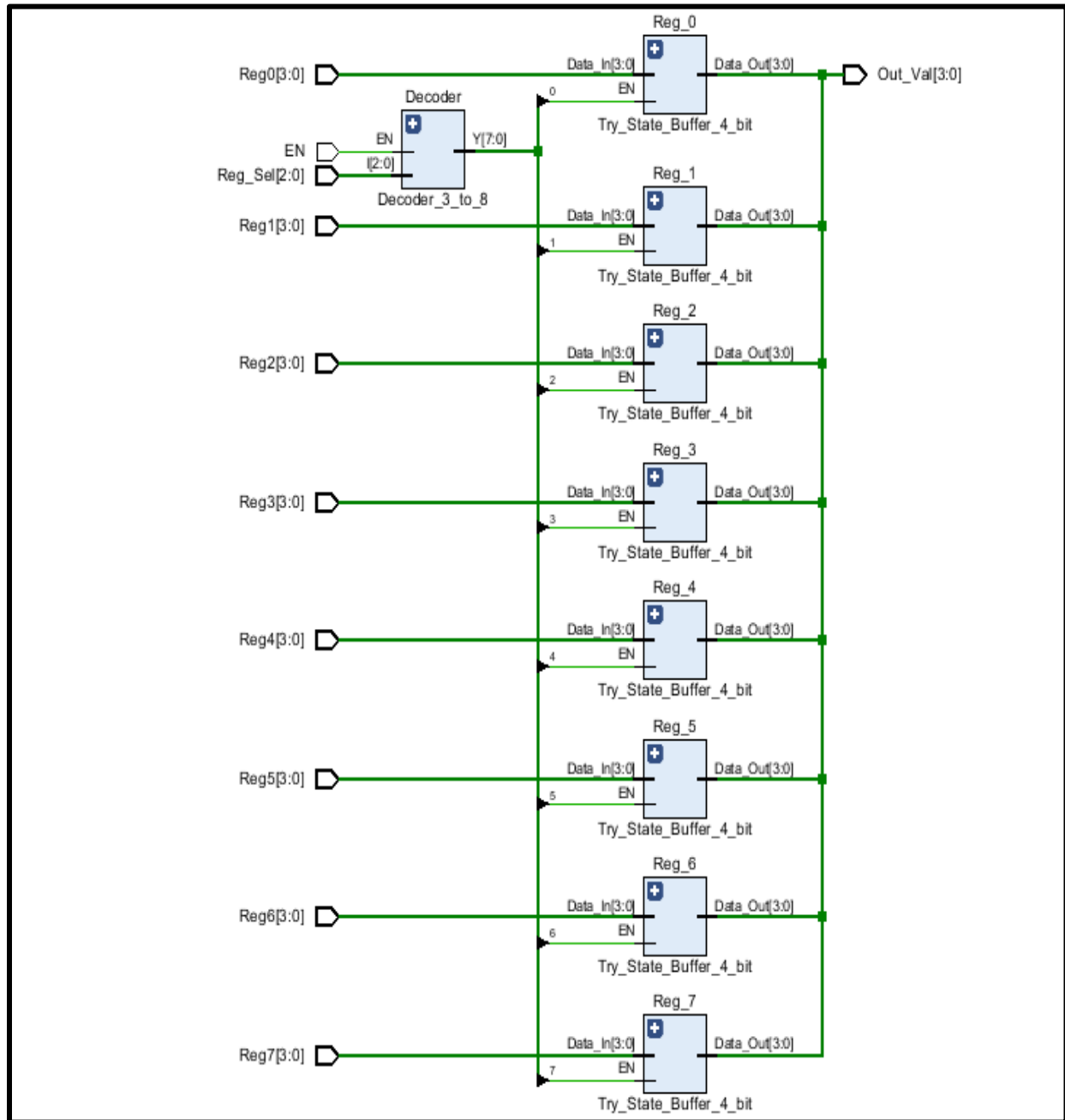
## RTL Schematic Diagram of 8-way 4-bit Multiplexer



### Code for 2-way 4-bit Multiplexer

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2_way_4_bit is
  Port ( Reg0 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg1 : in STD_LOGIC_VECTOR (3 downto 0);
        EN : in STD_LOGIC;
        Reg_Sel : in STD_LOGIC ;
        Out_Val : out STD_LOGIC_VECTOR (3 downto 0));
end Mux_2_way_4_bit;

architecture Behavioral of Mux_2_way_4_bit is
  --add a decoder to enable registers separately
  component Decoder_1_to_2
    Port ( I : in STD_LOGIC;
          EN : in STD_LOGIC;
          Y : out STD_LOGIC_VECTOR(1 downto 0));
  end component;

  --add a try state buffer to throw the correct input to common bus after enable
  --correct try state buffer
  component Try_State_Buffer_4_bit
    Port ( Data_In : in STD_LOGIC_VECTOR (3 downto 0);
          EN : in STD_LOGIC;
          Data_Out : out STD_LOGIC_VECTOR (3 downto 0));
  end component;

  Signal Common_Data_Bus : STD_LOGIC_VECTOR (3 downto 0);
  signal RegSel : STD_LOGIC_VECTOR (1 downto 0);

begin
  --decode the input register and select correct try state buffer
  Decoder: Decoder_1_to_2
    port map (
      I => Reg_Sel,
      EN => EN,
```

```

        Y => RegSel);
    Reg_0: Try_State_Buffer_4_bit
    port map(
        Data_In => Reg0,
        EN => RegSel(0),
        Data_Out => Common_Data_Bus );


    Reg_1: Try_State_Buffer_4_bit
    port map(
        Data_In => Reg1,
        EN => RegSel(1),
        Data_Out => Common_Data_Bus );

--output common bus
    Out_Val <= Common_Data_Bus;

end Behavioral;

```
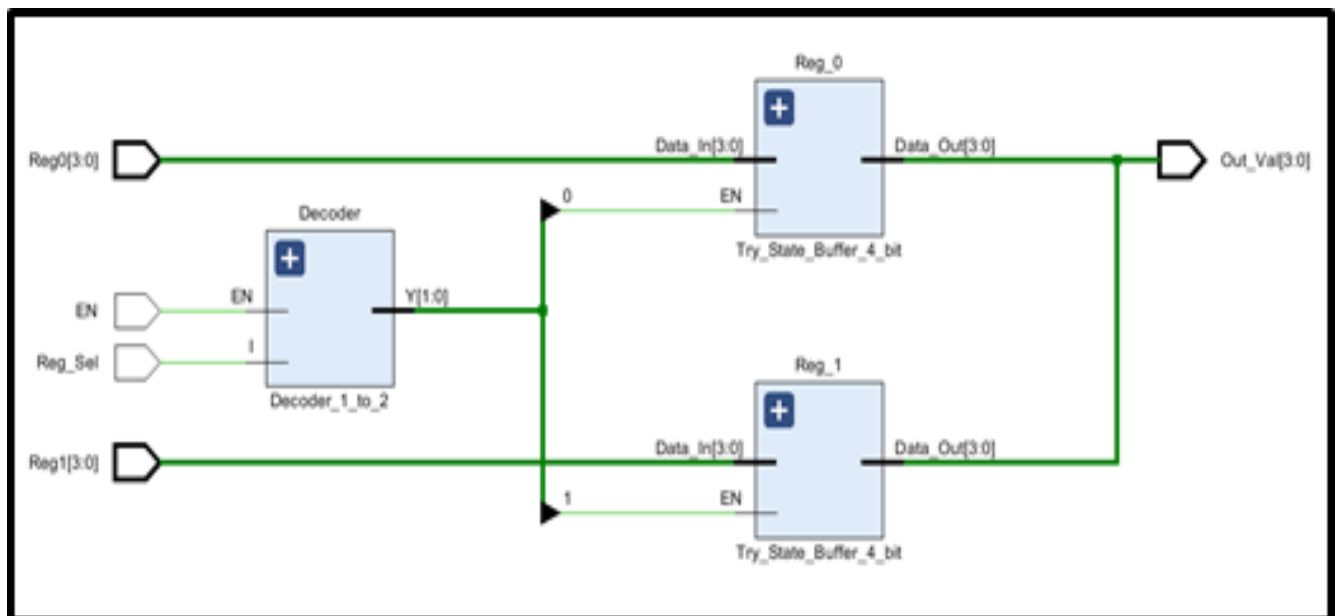
### RTL Schematic Diagram of 2-way 4-bit Multiplexer



## Code for 2-way 3-bit Multiplexer

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_2_way_3_bit is
    Port ( Reg0 : in STD_LOGIC_VECTOR (2 downto 0);
          Reg1 : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Reg_Sel : in STD_LOGIC ;
          Out_Val : out STD_LOGIC_VECTOR (2 downto 0));
end Mux_2_way_3_bit;

architecture Behavioral of Mux_2_way_3_bit is

    --add a decoder to enable registers separately
    component Decoder_1_to_2
        Port ( I : in STD_LOGIC;
              EN : in STD_LOGIC;
              Y : out STD_LOGIC_VECTOR(1 downto 0));
    end component;

    --add a try state buffer to throw the correct input to common bus after enable correct try state buffer
    component Try_State_Buffer_3_bit
        Port ( Data_In : in STD_LOGIC_VECTOR (2 downto 0);
              EN : in STD_LOGIC;
              Data_Out : out STD_LOGIC_VECTOR (2 downto 0));
    end component;

    Signal Common_Data_Bus : STD_LOGIC_VECTOR (2 downto 0);
    signal RegSel :STD_LOGIC_VECTOR (1 downto 0);

begin
    --decode the input register and select correct try state buffer
    Decoder: Decoder_1_to_2
        port map (
            I => Reg_Sel,
            EN => EN,
            Y => RegSel );

    Reg_0: Try_State_Buffer_3_bit
        port map(
            Data_In => Reg0,
            EN => RegSel(0),
            Data_Out => Common_Data_Bus );
```



```

Reg_1: Try_State_Buffer_3_bit
port map(
  Data_In => Reg1,
  EN => RegSel(1),
  Data_Out => Common_Data_Bus );

```

*--output common bus*

```

Out_Val <= Common_Data_Bus;


```

```

end Behavioral;

```
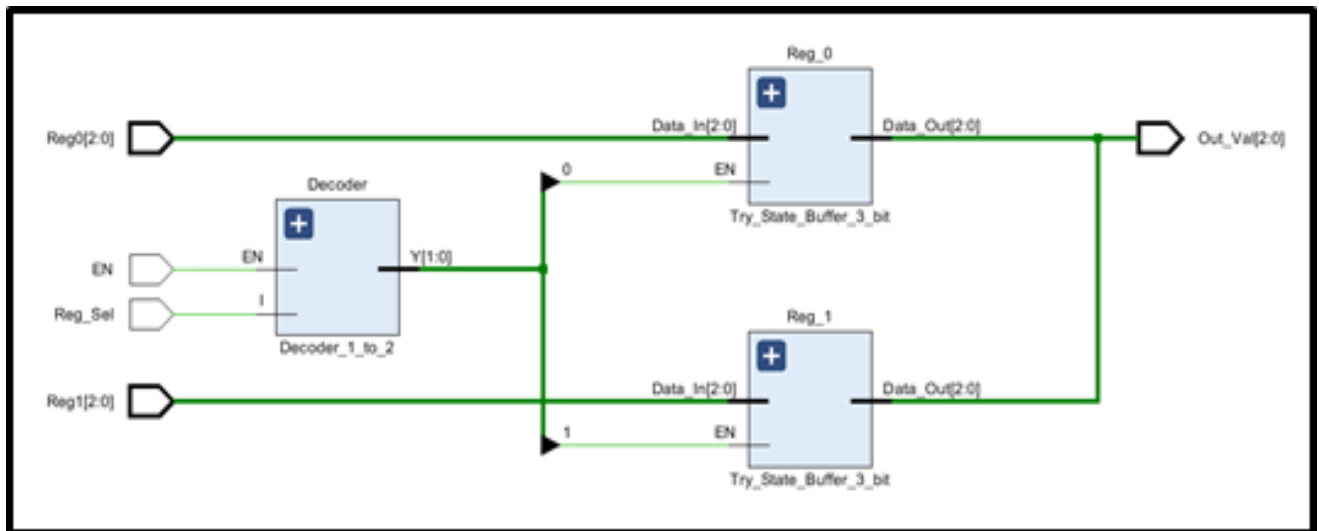
### RTL Schematic Diagram of 2-way 4-bit Multiplexer



## 5. Register Bank

8 Registers are used to create register bank and 3 to 8 decoder used to separate register addresses.

### VHDL Code for Register Bank

```
entity Register_Bank is
Port ( RegIn : in STD_LOGIC_VECTOR (3 downto 0);
      Clk : in STD_LOGIC;
      Reset : in STD_LOGIC;
      RegSel : in STD_LOGIC_VECTOR (2 downto 0);
      R0 : out STD_LOGIC_VECTOR (3 downto 0);
      R1 : out STD_LOGIC_VECTOR (3 downto 0);
      R2 : out STD_LOGIC_VECTOR (3 downto 0);
      R3 : out STD_LOGIC_VECTOR (3 downto 0);
      R4 : out STD_LOGIC_VECTOR (3 downto 0);
      R5 : out STD_LOGIC_VECTOR (3 downto 0);
      R6 : out STD_LOGIC_VECTOR (3 downto 0);
      R7 : out STD_LOGIC_VECTOR (3 downto 0));
end Register_Bank;

architecture Behavioral of Register_Bank is

component Reg
  Port ( D : in STD_LOGIC_VECTOR (3 downto 0);
        EN : in STD_LOGIC;
        Reset: in std_logic;
        Clk : in STD_LOGIC;
        Q : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Decoder_3_to_8
Port ( I : in STD_LOGIC_VECTOR (2 downto 0);
      EN : in STD_LOGIC;
      Y : out STD_LOGIC_VECTOR (7 downto 0));
end component;

  signal EnableReg : std_logic_vector(7 downto 0);

begin
  Decoder: Decoder_3_to_8
    port map( I => RegSel,
              EN => '1',
              Y => EnableReg);
```

#### Register\_0:Reg

```
port map( D => "0000",  
         EN => EnableReg(0),  
         Reset => Reset,  
         Clk => Clk,  
         Q => R0);
```

#### Register\_1:Reg

```
port map( D => RegIn,  
         EN => EnableReg(1),  
         Reset => Reset,  
         Clk => Clk,  
         Q => R1);
```

#### Register\_2:Reg

```
port map( D => RegIn,  
         EN => EnableReg(2),  
         Reset => Reset,  
         Clk => Clk,  
         Q => R2);
```

#### Register\_3:Reg

```
port map( D => RegIn,  
         EN => EnableReg(3),  
         Reset => Reset,  
         Clk => Clk,  
         Q => R3);
```

#### Register\_4:Reg

```
port map( D => RegIn,  
         EN => EnableReg(4),  
         Reset => Reset,  
         Clk => Clk,  
         Q => R4);
```

#### Register\_5:Reg

```
port map( D => RegIn,  
         EN => EnableReg(5),  
         Reset => Reset,  
         Clk => Clk,  
         Q => R5);
```

#### Register\_6:Reg

```
port map( D => RegIn,  
         EN => EnableReg(6),  
         Reset => Reset,
```

```

Clk => Clk,
Q => R6);

```

**Register\_7:Reg**

```

port map( D => RegIn,
          EN => EnableReg(7),
          Reset => Reset,
          Clk => Clk,
          Q => R7);


```

```

end Behavioral;

```
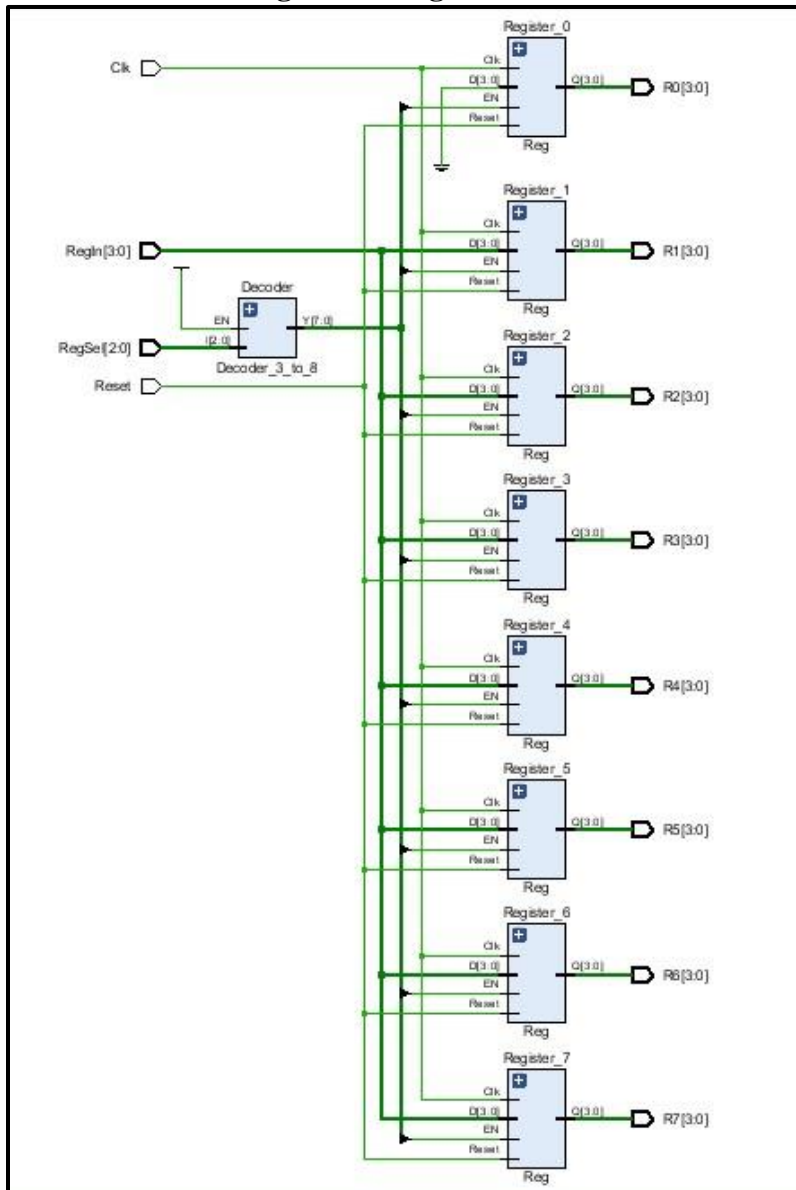
### RTL Schematic Diagram of Register Bank



## 6. Program ROM

A set of predefined instructions are going to be executed in the nano processor. The task is to obtain the sum of 1-3 umbers. The instructions are written in assembly language and they are stored in the ROM.


### Code for Program Rom

```
entity Prog_ROM is
  Port ( MemorySelect : in STD_LOGIC_VECTOR (2 downto 0);
        InstructionBus : out STD_LOGIC_VECTOR (11 downto 0));
end Prog_ROM;

architecture Behavioral of Prog_ROM is
  type rom_type is array (0 to 7) of std_logic_vector(11 downto 0);

  --a lookup table is used to store instructions
  signal ROM_bank : rom_type := (
    "101110000000", -- R7 <- 0
    "100010000011", -- R1 <- 3
    "100100000001", -- R2 <- 1
    "010100000000", --R2 <- Neg R2
    "001110010000", --R7 <- R7 + R1
    "000010100000", -- R1 <- R1 + R2
    "110010000110", -- If R1 0 jump to 6
    "110000000100" --If R0 jump to 4
  );
begin
  InstructionBus <= ROM_bank(to_integer(unsigned(MemorySelect)));
end Behavioral;
```

### RTL Schematic Diagram of Program ROM

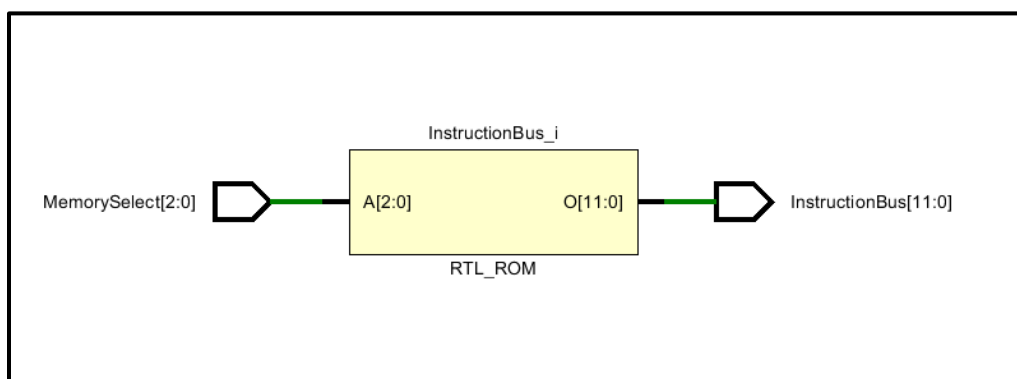

## 7. Instruction Decoder

Instruction decoder is the instruction fetching unit in that processor. In this unit mainly do following things. decoding the instruction, sending instruction signals to the relevant components, and putting data into the data busses. After decoding the instruction first that unit select the operation from the op code using a 2 to 4 decoder. Then relative to the ADD, NEG, MOVI, JZR operations, it gives the instructions to components and add data into busses

### Code for Instruction Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder is
    Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
          Reg_Chk_Jmp : in STD_LOGIC_VECTOR (3 downto 0);
          Load_Sel : out STD_LOGIC;
          Add_Sub_Sel : out STD_LOGIC;
          Jmp_Flag : out STD_LOGIC;
          Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
          Immediate_Val : out STD_LOGIC_VECTOR (3 downto 0);
          Reg_Sel_1 : out STD_LOGIC_VECTOR (2 downto 0);
          Reg_Sel_2 : out STD_LOGIC_VECTOR (2 downto 0);
          Address_Jmp : out STD_LOGIC_VECTOR (2 downto 0));
end Instruction_Decoder;

architecture Behavioral of Instruction_Decoder is
    --add a decoder to select the correct opcode
    component Decoder_2_to_4
        Port ( I : in STD_LOGIC_VECTOR (1 downto 0);
              EN : in STD_LOGIC;
              Y : out STD_LOGIC_VECTOR (3 downto 0));
    end component;

    Signal Add,Neg,Mov,JzR,Not_JzR: std_logic;
begin
    --decode the opcode
    Decoder : Decoder_2_to_4
        port map(
            I => Instruction(11 downto 10),
            EN => '1',
            Y(0) => Add, --if opcode is 00 then add will be 1
            Y(1) => Neg, --if opcode is 01 then Neg will be 1
            Y(2) => Mov, --if opcode is 10 then Mov will be 1
            Y(3) => JzR); --if opcode is 11 then JzR will be 1
```



## 8. NanoProcessor

### Code for NanoProcessor

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity NanoProcessor is
  Port ( Reset : in STD_LOGIC;
        Clk : in STD_LOGIC;
        Zero_Flag : out STD_LOGIC;
        Overflow_Flag : out STD_LOGIC;
        LED : out STD_LOGIC_VECTOR (3 downto 0);
        Carry_Out : out STD_LOGIC;
        SD_7 : out STD_LOGIC_VECTOR (6 downto 0));
end NanoProcessor;

architecture Behavioral of NanoProcessor is
  component Slow_Clk
    port( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
  end component;

  component ProgramCounter
    port( I_in : in STD_LOGIC_VECTOR (2 downto 0);
          Clk : in STD_LOGIC;
          Res : in STD_LOGIC;
          I_out : out STD_LOGIC_VECTOR (2 downto 0));
  end component;

  component Adder_3_bit
    Port ( TBA_in : in STD_LOGIC_VECTOR (2 downto 0);
          TBA_out : out STD_LOGIC_VECTOR (2 downto 0));
  end component;

  component Mux_2_way_3_bit
    Port ( Reg0 : in STD_LOGIC_VECTOR (2 downto 0);
          Reg1 : in STD_LOGIC_VECTOR (2 downto 0);
          EN : in STD_LOGIC;
          Reg_Sel : in STD_LOGIC ;
          Out_Val : out STD_LOGIC_VECTOR (2 downto 0));
  end component;

  component Prog_ROM
    Port ( MemorySelect : in STD_LOGIC_VECTOR (2 downto 0);
          InstructionBus : out STD_LOGIC_VECTOR (11 downto 0));
```



```

end component;

component Instruction_Decoder
  Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
        Reg_Chk_Jmp : in STD_LOGIC_VECTOR (3 downto 0);
        Load_Sel : out STD_LOGIC;
        Add_Sub_Sel : out STD_LOGIC;
        Jmp_Flag : out STD_LOGIC;
        Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
        Immediate_Val : out STD_LOGIC_VECTOR (3 downto 0);
        Reg_Sel_1 : out STD_LOGIC_VECTOR (2 downto 0);
        Reg_Sel_2 : out STD_LOGIC_VECTOR (2 downto 0);
        Address_Jmp : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Mux_2_way_4_bit
  Port ( Reg0 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg1 : in STD_LOGIC_VECTOR (3 downto 0);
        EN : in STD_LOGIC;
        Reg_Sel : in STD_LOGIC ;
        Out_Val : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Register_Bank
  Port ( RegIn : in STD_LOGIC_VECTOR (3 downto 0);
        Clk : in STD_LOGIC;
        Reset : in STD_LOGIC;
        RegSel : in STD_LOGIC_VECTOR (2 downto 0);
        R0 : out STD_LOGIC_VECTOR (3 downto 0);
        R1 : out STD_LOGIC_VECTOR (3 downto 0);
        R2 : out STD_LOGIC_VECTOR (3 downto 0);
        R3 : out STD_LOGIC_VECTOR (3 downto 0);
        R4 : out STD_LOGIC_VECTOR (3 downto 0);
        R5 : out STD_LOGIC_VECTOR (3 downto 0);
        R6 : out STD_LOGIC_VECTOR (3 downto 0);
        R7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Mux_8_way_4_bit
  Port ( Reg0 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg1 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg2 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg3 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg4 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg5 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg6 : in STD_LOGIC_VECTOR (3 downto 0);
        Reg7 : in STD_LOGIC_VECTOR (3 downto 0);

```

```

    EN : in STD_LOGIC;
    Reg_Sel : in STD_LOGIC_VECTOR (2 downto 0);
    Out_Val : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component Adder_Subtractor
    Port ( A : in STD_LOGIC_VECTOR (3 downto 0);
          B : in STD_LOGIC_VECTOR (3 downto 0);
          CalCtrl : in STD_LOGIC;
          C_out : out STD_LOGIC;
          Overflow : out STD_LOGIC;
          Zero : out STD_LOGIC;
          S : out STD_LOGIC_VECTOR (3 downto 0));
end component;

component LUT_16_7
    Port ( address : in STD_LOGIC_VECTOR (3 downto 0);
          data : Out STD_LOGIC_VECTOR (6 downto 0));
end component;

Signal Clk_out : std_logic;
Signal Ins_next, Ins_Current, Normal_Ins : std_logic_vector (2 downto 0);

Signal jump_flag, Add_Sub_Select, Load_Select : std_logic;
Signal Instruction : std_logic_vector (11 downto 0);
Signal Immediate_Value, Calculate_value : std_logic_vector (3 downto 0);
Signal Register_Enable, Num_1_Select, Num_2_Select, Jump_Address : std_logic_vector
(2 downto 0);

Signal Register_save_Value, R0,R1,R2,R3,R4,R5,R6,R7 : std_logic_vector (3 downto 0);

Signal Number1, Number2 : std_logic_vector (3 downto 0);
Signal C_out : std_logic; --carry out

begin
Clock :Slow_Clk port map(
    Clk_in => Clk,
    Clk_out => Clk_out);

Number1_select : Mux_8_way_4_bit port map(
    Reg0 => R0,
    Reg1 => R1,
    Reg2 => R2,
    Reg3 => R3,
    Reg4 => R4,
    Reg5 => R5,
    Reg6 => R6,

```

```

Reg7 => R7,
EN => '1',
Reg_Sel => Num_1_Select,
Out_Val => Number1);

```

**Number2\_select** : Mux\_8\_way\_4\_bit port map(

```

Reg0 => R0,
Reg1 => R1,
Reg2 => R2,
Reg3 => R3,
Reg4 => R4,
Reg5 => R5,
Reg6 => R6,
Reg7 => R7,
EN => '1',
Reg_Sel => Num_2_Select,
Out_Val => Number2);

```

**RegisterBank** : Register\_Bank port map(

```

RegIn => Register_save_Value,
Clk => Clk_out,
Reset => Reset,
RegSel => Register_Enable,
R0 => R0,
R1 => R1,
R2 => R2,
R3 => R3,
R4 => R4,
R5 => R5,
R6 => R6,
R7 => R7);

```

**ALU** : Adder\_Subtractor port map(

```

A => Number2,
B => Number1,
CalCtrl => Add_Sub_Select,
Overflow => Overflow_Flag,
Zero => Zero_Flag,
S => Calculate_value,
C_out => Carry_Out);

```

**InstructionDecoder** : Instruction\_Decoder port map(

```

Instruction => Instruction,
Reg_Chk_Jmp => Number1 ,
Load_Sel => Load_Select,
Add_Sub_Sel => Add_Sub_Select,
Jmp_Flag => jump_flag,

```

```

Reg_En => Register_Enable,
Immediate_Val => Immediate_Value,
Reg_Sel_1 => Num_1_Select,
Reg_Sel_2 => Num_2_Select,
Address_Jmp => Jump_Address);

```

**Multiplexer\_2\_way\_3\_bit**: Mux\_2\_way\_3\_bit port map(

```

Reg0 => Normal_ins,
Reg1 => Jump_Address,
EN => '1',
Reg_Sel => jump_flag,
Out_Val => Ins_next);

```

**Multiplexer\_2\_way\_4\_bit** : Mux\_2\_way\_4\_bit port map(

```

Reg0 => Calculate_value,
Reg1 => Immediate_Value,
EN => '1',
Reg_Sel => Load_Select,
Out_val => Register_save_Value);

```

**Display\_7\_segment** : LUT\_16\_7 port map(

```

address => R7,
data => SD_7);

```

**Programe\_ROM** : Prog\_ROM port map(

```

MemorySelect => Ins_Current,
InstructionBus => Instruction);

```

**ProgrameCounter** : ProgramCounter port map(

```

I_in=> Ins_next,
Clk => Clk_out,
Res => Reset,
I_out => Ins_Current);

```

**Adder\_3Bit** : Adder\_3\_bit port map(

```

TBA_in => Ins_Current,
TBA_out => Normal_Ins);

```

```

LED <= R7;


```

```

end Behavioral;

```

## Schematic diagram of NanoProcessor

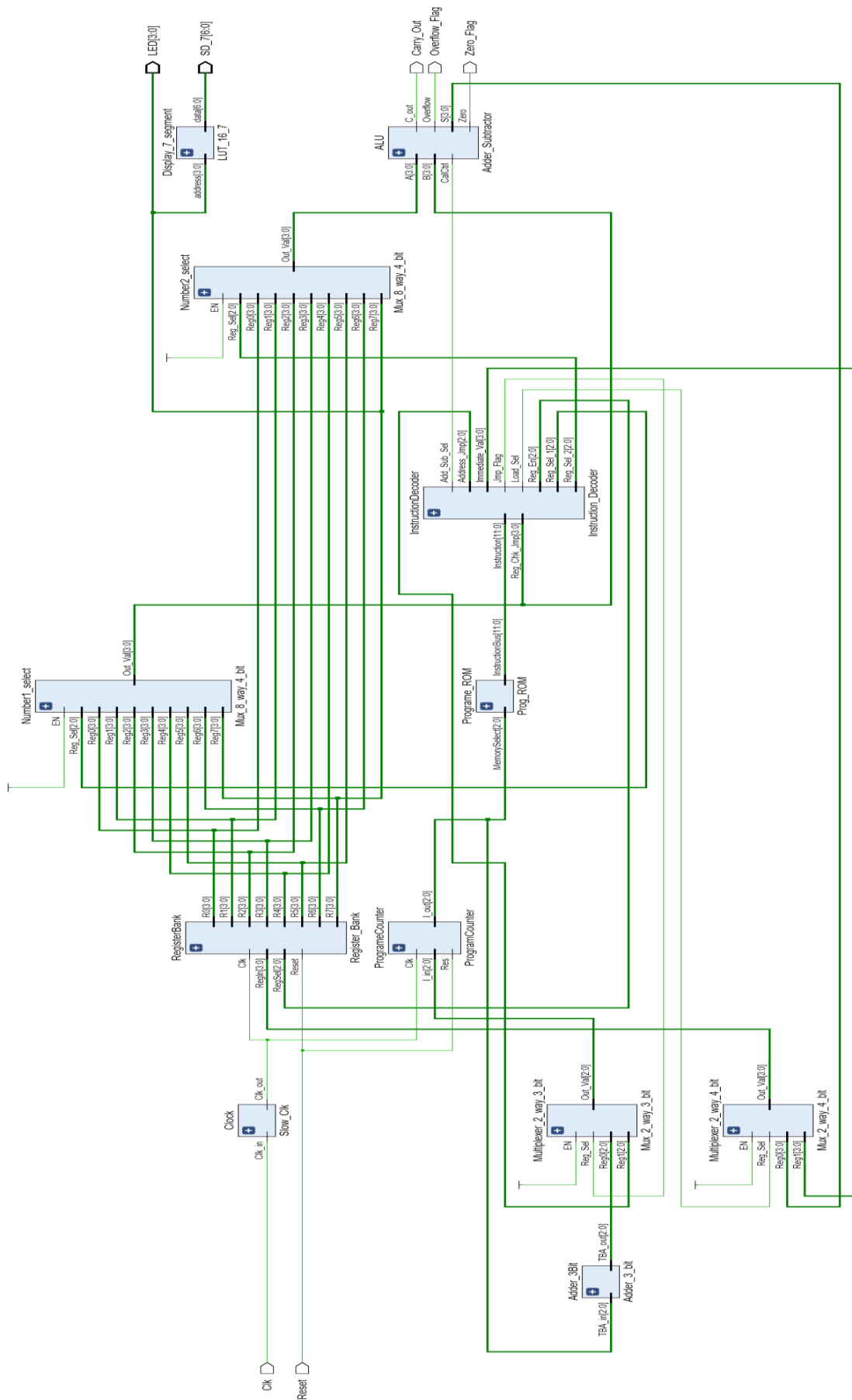

## Timing Diagrams

### 1. 4-bit Add/Subtract Unit

#### Simulation code for add/sub unit

```
entity Adder_Subtractor_Sim is
  -- port();
end Adder_Subtractor_Sim;

architecture Behavioral of Adder_Subtractor_Sim is
  component Adder_Subtractor

  port(
    A : in STD_LOGIC_VECTOR (3 downto 0);
    B : in STD_LOGIC_VECTOR (3 downto 0);
    CalCtrl : in STD_LOGIC;
    C_out : out STD_LOGIC;
    Overflow : out STD_LOGIC;
    Zero : out STD_LOGIC;
    S : out STD_LOGIC_VECTOR (3 downto 0));
  end component;

  signal A, B: std_logic_vector(3 downto 0);
  signal CalCtrl : std_logic;

  begin
    UUT : Adder_Subtractor port map(
      A => A,
      B => B,
      CalCtrl => CalCtrl,
      C_out => C_out,
      Overflow => Overflow,
      Zero => Zero,
      S => S
    );
    Sim : process
    begin
      CalCtrl <= '0';
      A(0) <= '1';
      A(1) <= '1';
      A(2) <= '1';
      A(3) <= '0';
      B(0) <= '1';
      B(1) <= '0';
      B(2) <= '0';
      B(3) <= '0';
```

```

wait for 100 ns;


CalCtrl <= '1';
A(0) <= '1';
A(1) <= '1';
A(2) <= '1';
A(3) <= '0';
B(0) <= '1';
B(1) <= '0';
B(2) <= '0';
B(3) <= '0';
wait for 100 ns;

CalCtrl <= '1';
A(0) <= '0';
A(1) <= '0';
A(2) <= '0';
A(3) <= '1';
B(0) <= '0';
B(1) <= '1';
B(2) <= '1';
B(3) <= '1';
wait for 100 ns;

CalCtrl <= '0';
A(0) <= '1';
A(1) <= '1';
A(2) <= '0';
A(3) <= '1';
B(0) <= '0';
B(1) <= '0';
B(2) <= '1';
B(3) <= '1';
wait for 100ns;
end process;
end Behavioral;

```

## Timing diagram of add/sub unit

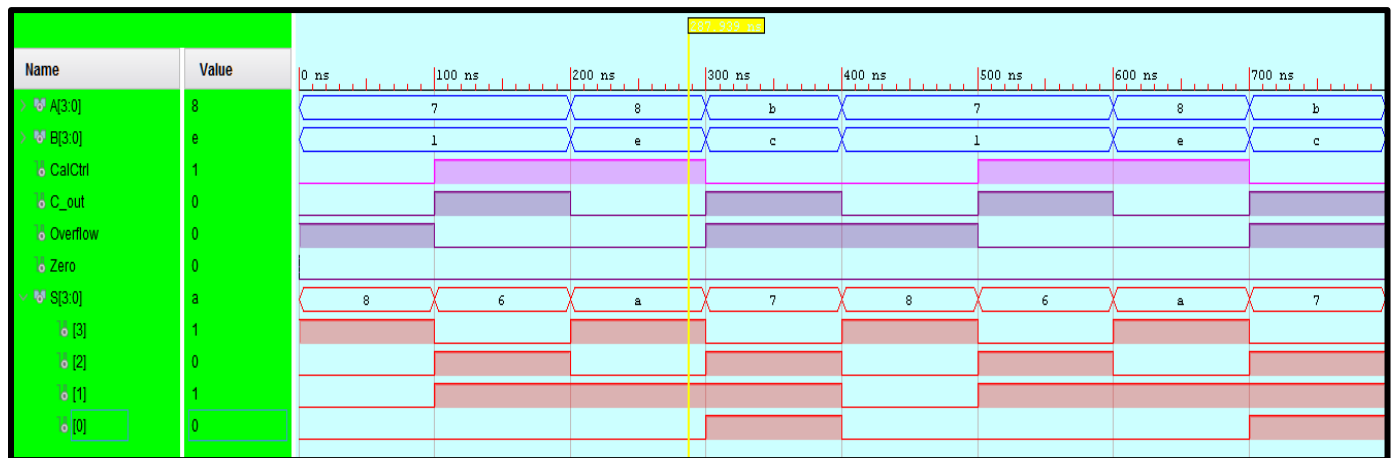

## 2. 3-bit Adder

### Simulation code for 3-bit adder

```
entity Adder_3_bit_sim is
-- Port ( );
end Adder_3_bit_sim;

architecture Behavioral of Adder_3_bit_sim is

component Adder_3_bit
port(
    TBA_in : in STD_LOGIC_VECTOR (2 downto 0);
    TBA_out : out STD_LOGIC_VECTOR (2 downto 0));
end component;

signal TBA_in : std_logic_vector(2 downto 0);
signal TBA_out : std_logic_vector(2 downto 0);

begin

uut: Adder_3_bit
port map(
    TBA_in => TBA_in,
    TBA_out => TBA_out);

Process
```



Begin

TBA\_in <= "011";

wait for 100ns;

TBA\_in <= "100";

wait for 100ns;


TBA\_in <= "111";

wait;

end process;

end Behavioral;

### Timing diagram for 3-bit adder

 

### 3. 3-bit Program Counter

#### Simulation code of 3-bit Program Counter

```
entity ProgramCounter_sim is
-- Port ( );
end ProgramCounter_sim;

architecture Behavioral of ProgramCounter_sim is

component ProgramCounter
    Port ( I_in : in STD_LOGIC_VECTOR (2 downto 0);
          Clk : in STD_LOGIC;
          Res : in STD_LOGIC;
          I_out : out STD_LOGIC_VECTOR (2 downto 0));
end component;

component Slow_Clk
    Port ( Clk_in : in STD_LOGIC;
          Clk_out : out STD_LOGIC);
end component;

signal I_in : STD_LOGIC_VECTOR (2 downto 0);
signal Clk, Slow_Clock : std_logic;
signal Res : STD_LOGIC:='0';
signal I_out : STD_LOGIC_VECTOR (2 downto 0);
constant clock_period: time:= 10ns;

begin

    uut: ProgramCounter
    port map(
        I_in => I_in,
        Clk => Slow_Clock,
        Res => Res,
        I_out => I_out);
    SlowClock: Slow_Clk port map(
        Clk_in => Clk,
        Clk_out => Slow_Clock);

    clock_process : process
    begin
        Clk <= '0';
        WAIT for clock_period/2;
        Clk <= '1';
        WAIT for clock_period/2;
    end process;
```

```

Sim :process
begin

  I_in <= "101";
  wait for 100 ns;

  I_in <= "100";
  wait for 100 ns;

  I_in <= "011";
  wait for 100 ns;


  Res <= '1';
  wait for 100 ns;
  Res <= '0';

  I_in <= "001";
  wait;

end process;
end Behavioral;

```
 
### Timing diagram of 3-bit Program Counter



#### 4. K-way b-bit Multiplexer

We use a decoder and try state buffers for all the k-way b-bit multiplexers. Here we show the time diagram of 8-way 4-bit Multiplexer. Other diagrams are same as this. First, we enter some values to registers of the multiplexer and after that we give different addresses to the multiplexer then the multiplexer gives the correct value in the given register.

##### Simulation code for 8-way 4-bit Multiplexer

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Mux_8_way_4_bit_Sim is
-- Port ();
end Mux_8_way_4_bit_Sim;

architecture Behavioral of Mux_8_way_4_bit_Sim is
component Mux_8_way_4_bit
    Port ( Reg0 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg1 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg2 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg3 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg4 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg5 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg6 : in STD_LOGIC_VECTOR (3 downto 0);
          Reg7 : in STD_LOGIC_VECTOR (3 downto 0);
          EN : in STD_LOGIC;
          Reg_Sel : in STD_LOGIC_VECTOR (2 downto 0);
          Out_Val : out STD_LOGIC_VECTOR (3 downto 0));
end component;

    Signal EN : std_logic;
    Signal Reg0, Reg1, Reg2, Reg3, Reg4, Reg5, Reg6, Reg7 ,Out_Val : std_logic_vector(3
downto 0);
    Signal Reg_Sel : std_logic_vector(2 downto 0);

begin
    UUT: Mux_8_way_4_bit port map(
        Reg0 => Reg0,
        Reg1 => Reg1,
        Reg2 => Reg2,
        Reg3 => Reg3,
        Reg4 => Reg4,
        Reg5 => Reg5,
        Reg6 => Reg6,
```

```
Reg7 => Reg7,  
EN => EN,  
Reg_Sel => Reg_Sel,  
Out_Val => Out_Val);
```

```
Sim:process
```

```
begin
```

```
    Reg0 <= "1111";  
    Reg1 <= "1110";  
    Reg2 <= "1101";  
    Reg3 <= "1100";  
    Reg4 <= "1011";  
    Reg5 <= "1010";  
    Reg6 <= "1001";  
    Reg7 <= "1000";  
    EN <= '1';
```

```
    Reg_Sel <= "011";  
    wait for 100ns;
```

```
    Reg_Sel <= "000";  
    wait for 100ns;
```

```
    Reg_Sel <= "101";  
    wait for 100ns;
```

```
    Reg_Sel <= "010";  
    wait for 100ns;
```

```
    Reg_Sel <= "100";  
    wait for 100ns;
```


```
    Reg_Sel <= "110";  
    wait for 100ns;
```

```
    Reg_Sel <= "001";  
    wait for 100ns;
```

```
    Reg_Sel <= "111";  
    wait;  
end process;
```

```
end Behavioral;
```
 
## Timing diagram of 8-way 4-bit Multiplexer



## 5. Register Bank

### Simulation code for Register Bank

```

entity Reg_Bank_Sim is
-- Port ();
end Reg_Bank_Sim;

architecture Behavioral of Reg_Bank_Sim is
component Register_Bank
    Port ( RegIn : in STD_LOGIC_VECTOR (3 downto 0);
          Clk : in STD_LOGIC;
          Reset : in STD_LOGIC;
          RegSel : in STD_LOGIC_VECTOR (2 downto 0);
          R0 : out STD_LOGIC_VECTOR (3 downto 0);
          R1 : out STD_LOGIC_VECTOR (3 downto 0);
          R2 : out STD_LOGIC_VECTOR (3 downto 0);
          R3 : out STD_LOGIC_VECTOR (3 downto 0);
          R4 : out STD_LOGIC_VECTOR (3 downto 0);
          R5 : out STD_LOGIC_VECTOR (3 downto 0);
          R6 : out STD_LOGIC_VECTOR (3 downto 0);
          R7 : out STD_LOGIC_VECTOR (3 downto 0));
end component;

```

```
signal Clk, Reset : std_logic;
signal RegIn, R0, R1, R2, R3, R4, R5, R6, R7 : std_logic_vector(3 downto 0);
signal RegSel : std_logic_vector(2 downto 0);
CONSTANT clock_period : TIME := 10ns;
```

```
begin
```

```
UUT: Register_Bank
```

```
port map(
```

```
    RegIn => RegIn,
    Clk => Clk,
    Reset => Reset,
    RegSel => RegSel,
    R0 => R0,
    R1 => R1,
    R2 => R2,
    R3 => R3,
    R4 => R4,
    R5 => R5,
    R6 => R6,
    R7 => R7);
```

```
clock_process : PROCESS
```

```
    BEGIN
```

```
        Clk <= '0';
```

```
        WAIT FOR clock_period/2;
```

```
        Clk <= '1';
```

```
        WAIT FOR clock_period/2;
```

```
    END PROCESS;
```

```
sim : PROCESS
```

```
    BEGIN
```

```
        Reset <= '1';
```

```
        WAIT FOR 100ns;
```

```
        Reset <= '0';
```

```
        RegIn <= "0010";
```

```
        RegSel <= "000";
```

```
        WAIT FOR 100ns;
```

```
        RegIn <= "0011";
```

```
        RegSel <= "001";
```

```
        WAIT FOR 100ns;
```

```
        RegIn <= "0100";
```

```
        RegSel <= "010";
```

```
        WAIT FOR 100ns;
```

```

RegIn <= "0101";
RegSel <= "011";
WAIT FOR 100ns;

RegIn <= "0111";
RegSel <= "100";
WAIT FOR 100ns;

RegIn <= "1000";
RegSel <= "101";
WAIT FOR 100ns;


RegIn <= "1010";
RegSel <= "110";
WAIT FOR 100ns;

RegIn <= "1001";
RegSel <= "111";

WAIT;
END PROCESS;
END Behavioral;

```

### Timing diagram of Register Bank

 



## 6. Program ROM

### Simulation code for Program ROM

```
entity Program_ROM_sim is
-- Port ();
end Program_ROM_sim;

architecture Behavioral of Program_ROM_sim is
component Program_ROM
    Port ( MemorySelect : in STD_LOGIC_VECTOR (2 downto 0);
          InstructionBus : out STD_LOGIC_VECTOR (11 downto 0));
end component;

signal MemorySelect : STD_LOGIC_VECTOR (2 downto 0);
signal InstructionBus : STD_LOGIC_VECTOR (2 downto 0);

begin

uut: Program_ROM
    port map(
        MemorySelect => MemorySelect,
        InstructionBus => InstructionBus
    );

sim:process

begin

    MemorySelect <= "100";
    wait for 100ns;

    MemorySelect <= "001";
    wait for 100ns;


    MemorySelect <= "111";
    wait for 100ns;

    MemorySelect <= "011";
    wait;

end process;

end Behavioral;
```

## Timing diagram of Program ROM

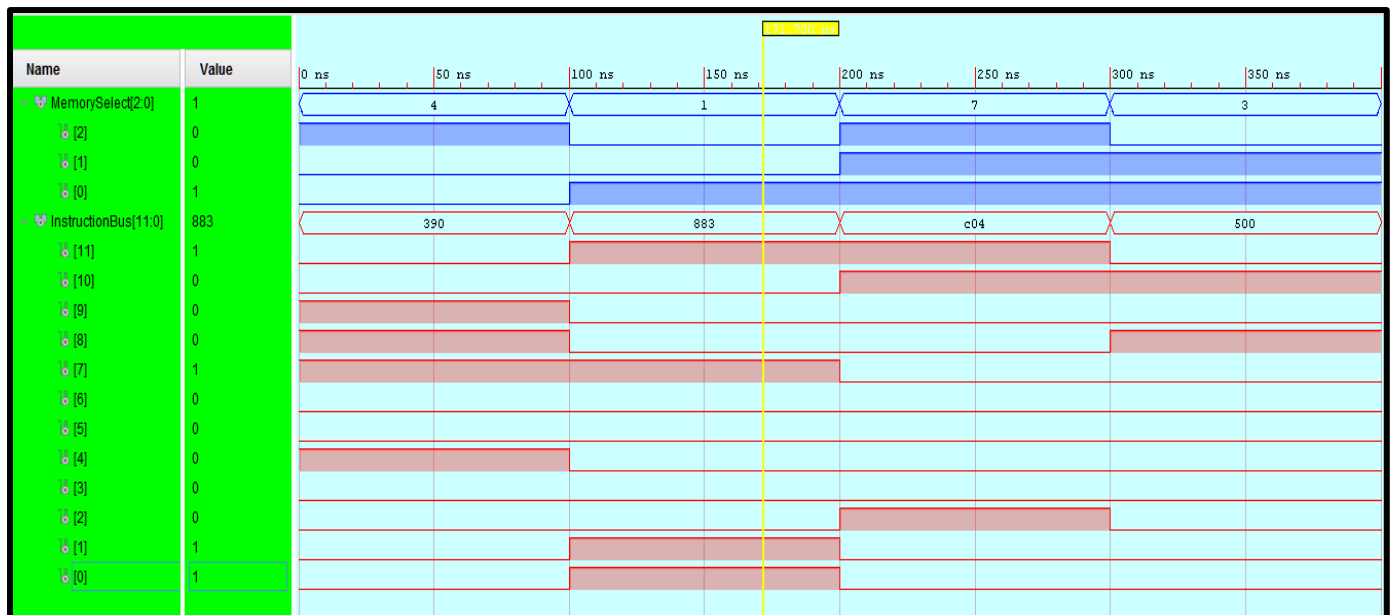

## 7. Instruction Decoder

Instruction Decoder was simulated by giving 4 different instructions to the Instruction Decoder. The instruction providing part of the simulation file is follows.

### Simulation code for Program Instruction Decoder

```
library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity Instruction_Decoder_Sim is
-- Port ();
end Instruction_Decoder_Sim;

architecture Behavioral of Instruction_Decoder_Sim is
component Instruction_Decoder
Port ( Instruction : in STD_LOGIC_VECTOR (11 downto 0);
      Reg_Chk_Jmp : in STD_LOGIC_VECTOR (3 downto 0);
      Load_Sel : out STD_LOGIC;
      Add_Sub_Sel : out STD_LOGIC;
      Jmp_Flag : out STD_LOGIC;
      Reg_En : out STD_LOGIC_VECTOR (2 downto 0);
      Immediate_Val : out STD_LOGIC_VECTOR (3 downto 0);
      Reg_Sel_1 : out STD_LOGIC_VECTOR (2 downto 0);
```

```

    Reg_Sel_2 : out STD_LOGIC_VECTOR (2 downto 0);
    Address_Jmp : out STD_LOGIC_VECTOR (2 downto 0));

end component;


Signal Load_Sel, Add_Sub_Sel, Jmp_Flag : std_logic;
Signal Reg_En, Reg_Sel_1, Reg_Sel_2, Address_Jmp : std_logic_vector(2 downto 0);
Signal Reg_Chk_Jmp, Immediate_Val : std_logic_vector(3 downto 0);
Signal Instruction : std_logic_vector( 11 downto 0);

begin
    UUT: Instruction_Decoder port map(
        Instruction => Instruction,
        Reg_Chk_Jmp => Reg_Chk_Jmp,
        Load_Sel => Load_Sel,
        Add_Sub_Sel => Add_Sub_Sel,
        Jmp_Flag => Jmp_Flag,
        Reg_En => Reg_En,
        Immediate_Val => Immediate_Val,
        Reg_Sel_1 => Reg_Sel_1,
        Reg_Sel_2 => Reg_Sel_2,
        Address_Jmp => Address_Jmp);

    sim :process
    begin
        --Assembly instruction is          MOVI R4, 6 ; R1 <- 6
        Instruction <= "101000000110";
        wait for 100ns;
        --Assembly instruction is          MOVI R2, 2 ; R1 <- 2
        Instruction <= "100100000010";
        wait for 100ns;
        --Assembly instruction is          NEG R2 ; R2 <- -R2
        Instruction <= "010100000000";
        wait for 100ns;
        --Assembly instruction is          ADD R4,R2 ; R4 <- R4 + R2
        Instruction <= "001000100000";
        wait for 100ns;
        --Assembly instruction is          JZR R2,7 ; If R2 = 0 jump to line 7
        Instruction <= "110100000111";
        Reg_Chk_Jmp <= "1110";
        wait for 100ns;
        --Assembly instruction is          JZR R0,4 ; If R0 = 0 jump to line 4
        Instruction <= "110000000100";
        Reg_Chk_Jmp <= "0000";
        wait;
    end process;
end Behavioral;

```
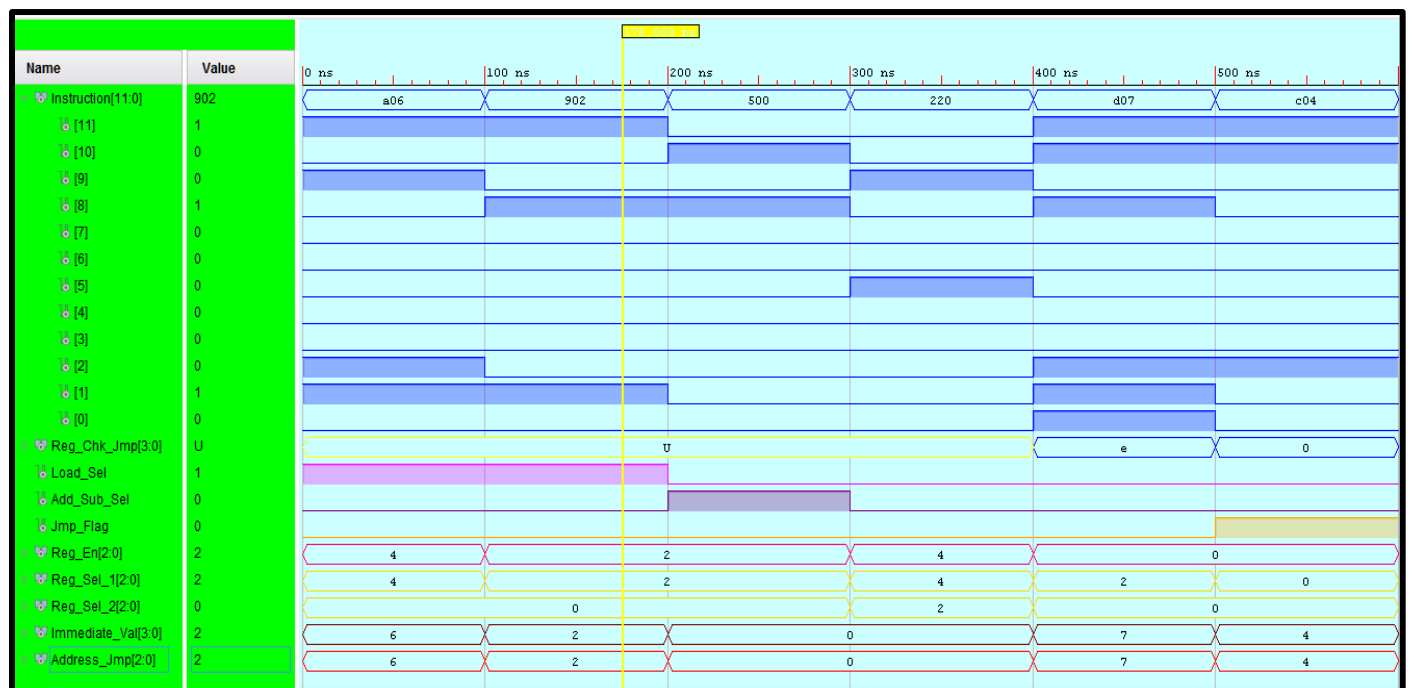
## Timing diagram of Program Instruction Decoder



## 8. NanoProcessor

### Simulation Code for NanoProcessor

```

entity NanoProcessorSim is
-- Port ( );
end NanoProcessorSim;

architecture Behavioral of NanoProcessorSim is
component NanoProcessor
port( Reset : in std_logic;
      Clk : in std_logic;
      Zero_Flag : out std_logic;
      Overflow_Flag : out std_logic;
      Carry_Out : out std_logic;
      LED : out STD_LOGIC_VECTOR (3 downto 0);
      SD_7 : out std_logic_vector( 6 downto 0));
end component;

Signal Reset, Clk, Zero_Flag, Overflow_Flag, Carry_Out: std_logic;
Signal SD_7_display: std_logic_vector (6 downto 0);
Signal LED: std_logic_vector (3 downto 0);
constant clock_period : time := 10ns;

```

```


begin
  UUT: NanoProcessor port map(
    Reset => Reset,
    Clk => Clk,
    Zero_Flag => Zero_Flag,
    Overflow_Flag => Overflow_Flag,
    Carry_Out => Carry_Out,
    LED => LED,
    SD_7 => SD_7_display);

  clock_process: process
  begin
    Clk <= '0';
    wait for clock_period/2;
    Clk <= '1';
    wait for clock_period/2;
  end process;

  Sim : process
  begin
    Reset <= '1';
    wait for 100ns;
    Reset <= '0';
    wait;
  end process;
end Behavioral;

```

## Timing Diagram of NanoProcessor

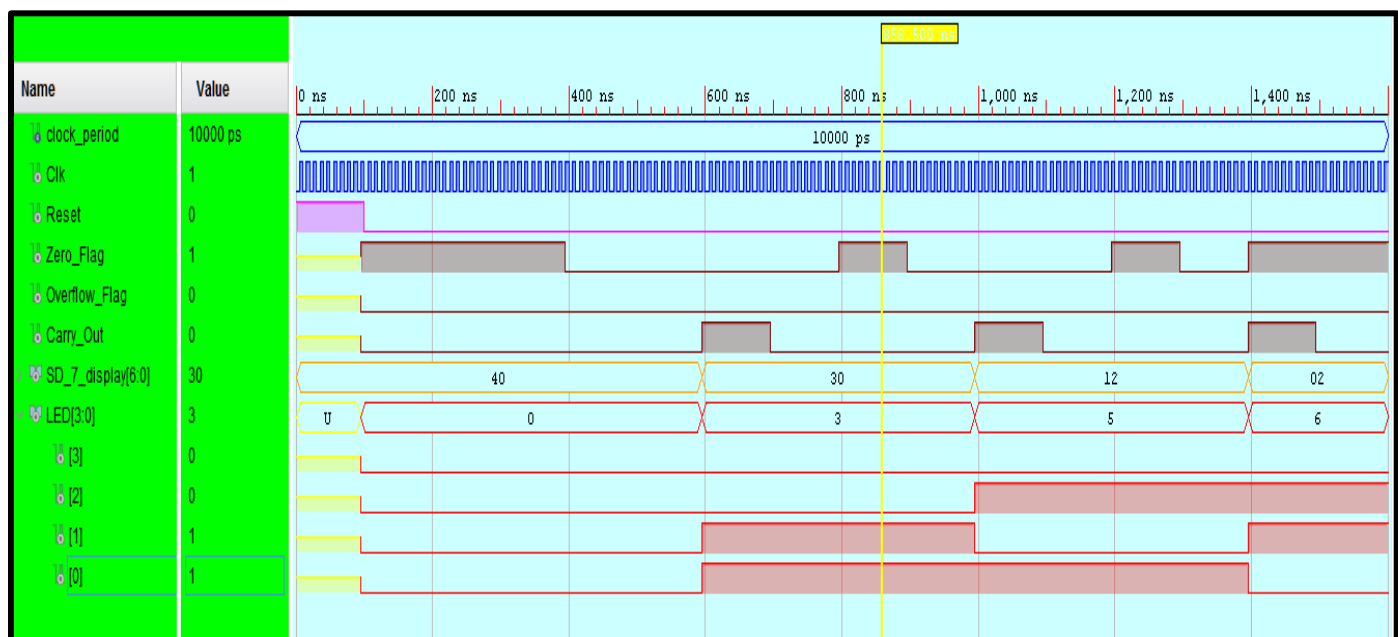

## Conclusion

- It is more apt to design the program counter using D flip flops since it needs to reset to 0 when required.
- MUX with tri state buffers are better than traditional MUX due to the reduction of unnecessary connections. At the same time, it makes the code more readable and understandable.
- The heavy usage of wires all around the circuit is mitigated through the usage of 3,4 and 12-bit buses.
- Instruction decoder is the most important component in the project as it stores all the machine language instructions of the processor.

## Contribution of Members

As mentioned in the Lab this is a group project then we divide main components between three group members. After creating components, all of us create the Nano Processor by connecting predesigned components together and simulate it. Finally Code the constraint file and generate the bitstream.

1. R.A.N. Sankalana	<ul style="list-style-type: none"><li>• 4 - bit Add/Sub unit</li><li>• Register bank</li></ul>
2. M.M. Poorna S. Cooray	<ul style="list-style-type: none"><li>• 3-bit adder</li><li>• 3-bit counter</li><li>• Program ROM</li></ul>
3. H.D.S. Vidulanka 4.	<ul style="list-style-type: none"><li>• Instruction Decoder,</li><li>• K-way b-bit mux</li></ul>